

Circuits and Systems 2CJ4

Lab 4

Jenisha Thevarajah – C01 – 400473218

Nandha Dileep – C01 – 400437930

Set 4 Laboratory Experiment

1. Given the circuit in Fig. 9, calculate the period T and frequency f of the oscillator.

Period:

$$T = R_1 C \left(\ln \frac{V_{sat}^+ - V_{th2}}{V_{sat}^+ - V_{th1}} + \ln \frac{V_{sat}^- - V_{th1}}{V_{sat}^- - V_{th2}} \right)$$

$$V_{th1} = \frac{R_3}{R_2 + R_3} \cdot (V_{sat}^+)$$

$$= \frac{1}{22+1} \cdot (5)$$

$$= \frac{5}{23} = 0.217$$

$$50 \times 10^3 \quad 100 \times 10^{-9}$$

$$V_{th2} = \frac{R_3}{R_2 + R_3} \cdot (V_{sat}^-)$$

$$= \frac{1}{23} \text{ (s)}$$

$$= \frac{-5}{23} = -0.217$$

$$T = 50 \times 100 \left(\ln \frac{5 - (-0.217)}{5 - 0.217} + \ln \left(\frac{(-5) - (-0.217)}{-5 - (-0.217)} \right) \right)$$

$$= (50 \times 10^3) \times (100 \times 10^{-9}) (0.081 + 0.081)$$

$$T = 869.08 \times 10^{-6} \text{ s}$$

$$= 0.869 \text{ ms}$$

Frequency:

$$f = \frac{1}{T} = \frac{1}{869.08 \times 10^{-6}} = 1150.64 \text{ Hz}$$

Figure 1: Analytical Calculations

2. Build the circuit in Fig. 9 and plot the voltage of the capacitor and the output voltage with respect to time (assuming $V_{sat} = \pm 5V$). Measure the time period T using the Analog Discovery 2 and compare it to the theoretical result.

Figure 2: Relaxation Oscillator Circuit


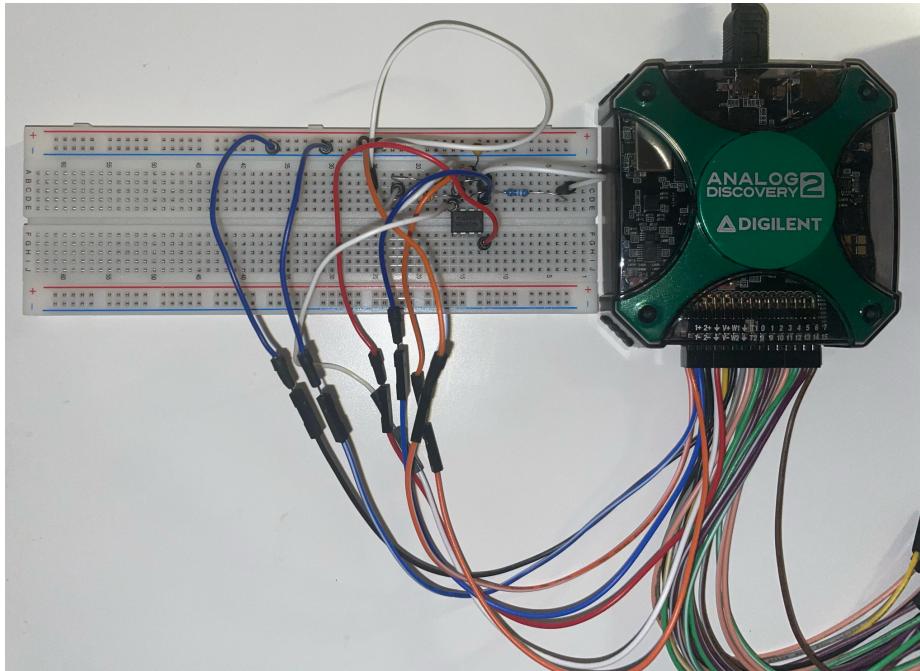


Figure 3: AD2 Measurement of $v_c(t)$, $v_{out}(t)$, and its Period

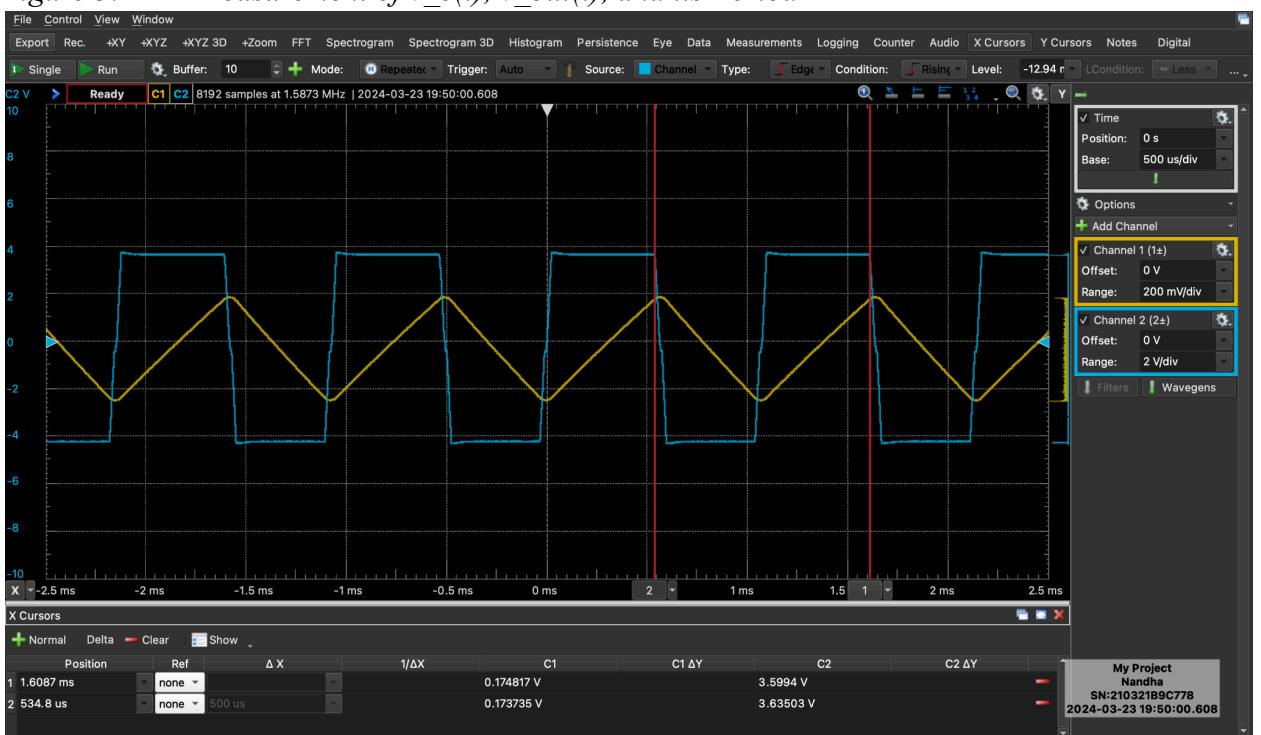

$$\begin{aligned}
T &= 1.6087 \text{ ms} - 534.8 \mu\text{s} \\
&= (1.6087 \times 10^{-3}) - (534.8 \times 10^{-6}) \\
&= 1.0739 \text{ ms}
\end{aligned}$$

Percent Error:

$$\begin{aligned}
\% \text{ Error} &= \frac{\text{Observed Value} - \text{True Value}}{\text{True Value}} \times 100\% \\
&= \frac{(1.0739 \times 10^{-3}) - (869.08 \times 10^{-6})}{869.08 \times 10^{-6}} \times 100\% \\
&= 23.57\%
\end{aligned}$$

Comparison:

The AD2 measurement of the period of the output voltage was 1.0739 ms, while the theoretical value was 869.08 μ s, resulting in a percent error of 23.57%, indicating close proximity between experimental and theoretical values; potential discrepancies may stem from factors like internal resistance within the breadboard and environmental conditions affecting the circuit. Additionally, the plot graph of $v_c(t)$ forming a triangular wave and $v_{out}(t)$ resembling a square wave confirms the functionality of a relaxation oscillator, as the capacitor charging and discharging cycles in the circuit generate a triangular waveform at $v_c(t)$, while the operational amplifier's saturation behavior ensures the output waveform $v_{out}(t)$ closely resembles a square wave.

3. Can you build a circuit by using another Op-Amp LM358P to generate a triangular output? Explain.

Yes, it is possible to build a circuit to generate a triangular output by using the other Op-Amp LM358P to create an integrator. Since, the $v_{out}(t)$ generates a square wave due to the saturation behavior, the integrator is able to transform the square wave into a triangular wave.

Essentially, the output voltage of the relaxation oscillator would be the input that is attached to a resistor which is connected to the negative input pin of the op-amp. Additionally, a capacitor would also be attached to the negative input pin and the output pin of the op-amp. The positive input pin of the op-amp would be grounded.